

Simulation Low Pass Filter

Abhishek Amit Raje

November 2023

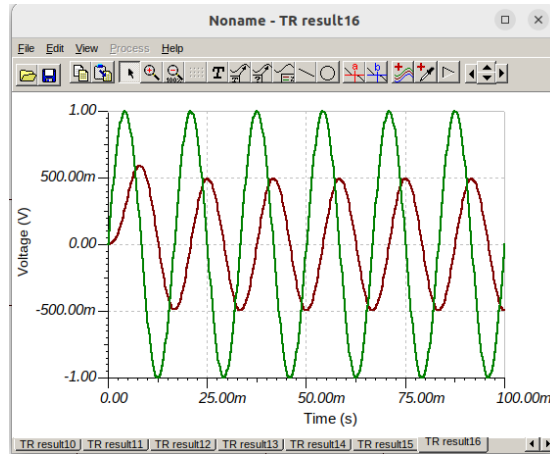


Figure 1: Input-output Graph at $f = 60$ Hz

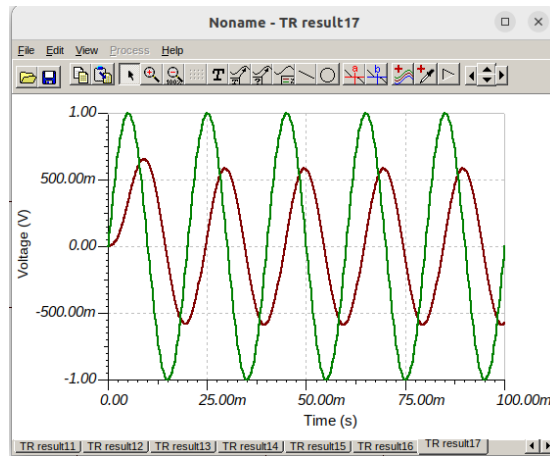


Figure 2: Input-output Graph at $f = 50$ Hz

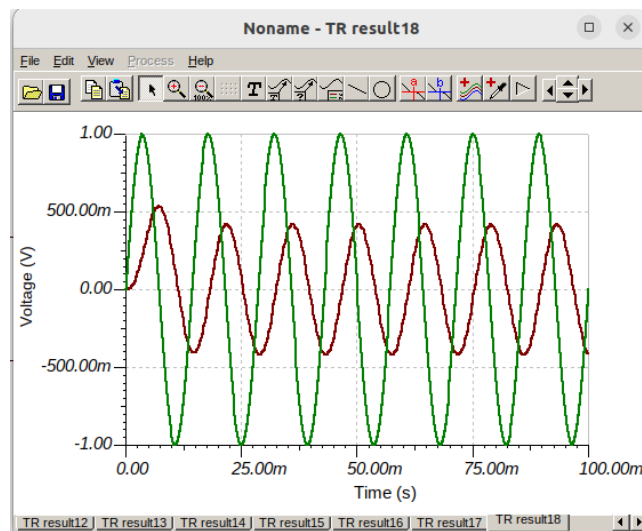


Figure 3: Input-output Graph at $f = 70$ Hz